

HW#2a

1. Construct an NXOR gate by interconnecting buffers and inverters.
2. Implement the following expression $F=AB'+C'D$ with
 - a) NAND-NAND gates
 - b) NOR-NOR gates